

Introduction

$$\text{CPU Time} = \text{Instruction Count} \times \text{CPI} \times \text{Clock Cycle Time}$$


- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - A simplified version → 在一个周期
 - A more realistic pipelined version → 在多个周期

Basic MIPS Architecture

- We have known the instructions a CPU should execute, we'll design a simple CPU that executes:
 - basic math (add, sub, and, or, slt)
 - memory access (lw and sw)
 - branch and jump instructions (beq and j)

Implement overview

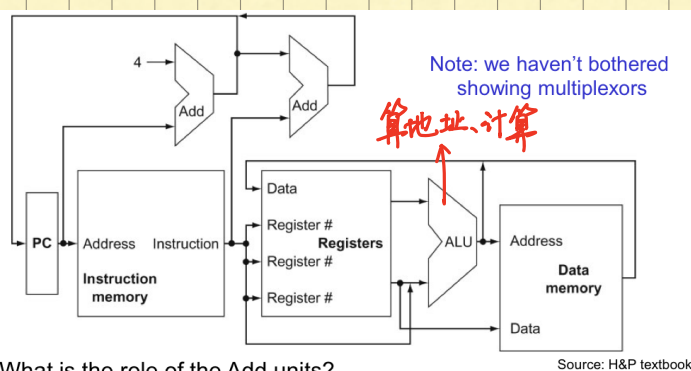- We need memory
 - to store instructions
 - to store data
 - for now, let's make them separate units
- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
 - use the program counter (PC) to pull instruction out of instruction memory
 - read register values



- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit

Logic Design Basic

- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational element
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information


Instruction memory 和 data memory 实际上是CPU中的cache, 便于快速取指令和数.

Combinational Elements


- And gate
 - $Y = A \& B$




- Adder
 - $Y = A + B$

 

- Multiplexer
 - $Y = S ? 1 : 0$

 


- Arithmetic/Logic Unit
 - $Y = F(A, B)$

 


State (sequential) Elements

 - State element
 - The state element has a pre-stored state
 - It has some internal storage
 - Has at least two inputs and one output (e.g. D-type flip-flop):
 - The data to be written into the element
 - The clock which determines when the data is written
 - The output: the value that was written in earlier cycle
 - Examples: register and memory




State Elements with write control

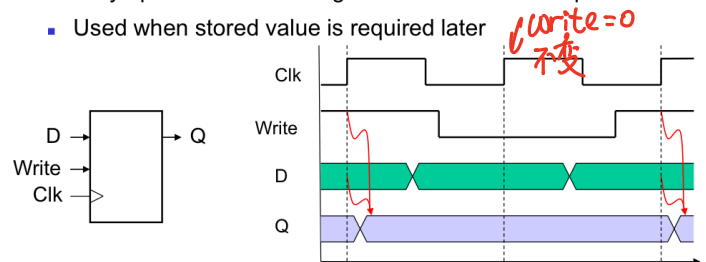- Register without write control (e.g. program counter)
 - Uses a clock signal to determine when to update
 - Edge-triggered: update when Clk changes from 0 to 1
- Register with write control (e.g. data memory/register)
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later



Instruction Memory

 - A state element with
- Input: InstructionAddress (32-bit), clock
- Output: Instructions (32-bit)
- State: the instructions stored in the memory ($n \times 32$ -bit)
- Why no control signals?
 - No write operation
 - Every clock read an instruction




输入指令地址 输出指令。

不需要使能信号, 因为没有写操作。
每个时钟都读一个指令。

Data Memory

 - A state element with
- Input: Address (32-bit), Write-in data (32-bit), MemWrite (1-bit), MemRead (1-bit), clock
- Output: Read-out data (32-bit)
- State: the data stored in the memory ($n \times 32$ -bit)



MemWrite 只当 store 指令时为 1
MemRead 只当 load 指令时为 1。

Registers

- State element
- Input: three register numbers (5-bit *3), write-in data (32-bit), RegWrite (1-bit)
- Output: readdata1 (32-bit), readdata 2 (32-bit)
- State: 32 * 32-bit data


Register 的编号是 5 位, 因为只有 32 个 register



32x32 bit 的数据

Register Read

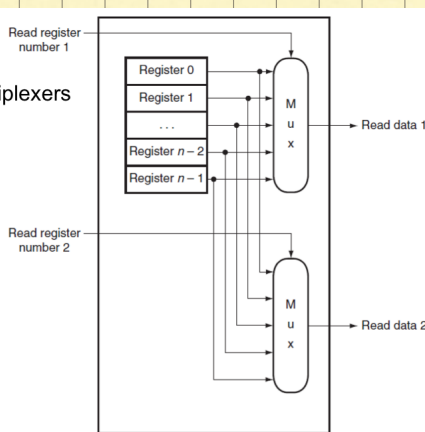
- Input: two addresses
- Output: two data
- Key component: two multiplexers



rs, 比两个寄存器, 有时要同时读.

Register Write

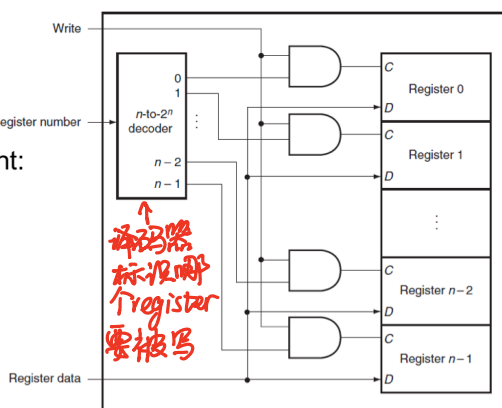- Input:
 - write control
 - address
 - writing data
- Key component:
 - decoder





rd 一个寄存器

Clocking Methodology 钟控方法

- Defines when signals can be read and when they can be written
- Edge-triggered clocking: all state changes occur on a clock edge.
- Clock time > the time needed for signals to propagate from SE1 through combinatorial element to SE2
- A state element can be read and written in the same clock cycle without creating a race, but the clock cycle should be long enough

所有状态的改变都发生在上升/下降沿.

 

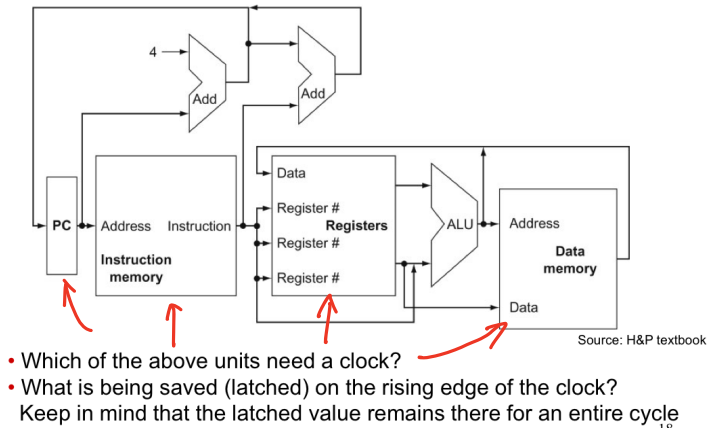

- Which of the above units need a clock?
- What is being saved (latched) on the rising edge of the clock?
Keep in mind that the latched value remains there for an entire cycle


在时钟上升沿时储存:

- ① PC的新值
- ② Register的新data

Fetch Instructions

- The instruction is fetched from I-mem and the PC is added by 4
- Components: program counter, instruction memory, adder
 - The PC is a 32-bit register, written at every positive edge of the clock, thus, it does not need write control signal.

PC在每个上升沿被写, 不需要写控制信号.

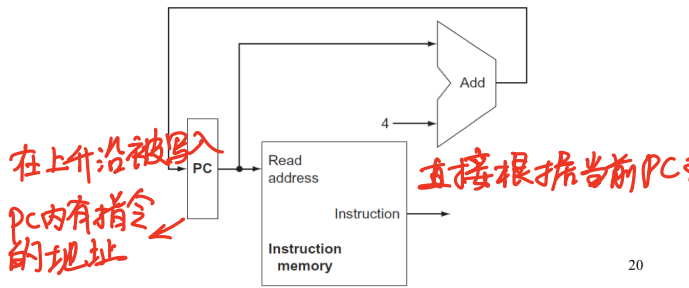

在上升沿被写入
PC内有指令的地址


直接根据当前PC的值获取指令.

直到最终将data写回register时
才在时钟上升沿操作.

Implementing R-type Instructions

- Instructions of the form add \$t1, \$t2, \$t3
- Explain the role of each signal


表示ALU做什么操作

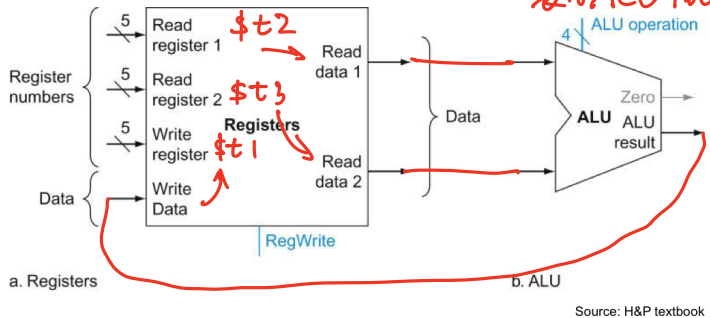

Implementing Loads / Stores

- Instructions of the form lw \$t1, 8(\$t2) and sw \$t1, 8(\$t2)

获取指令在上升沿

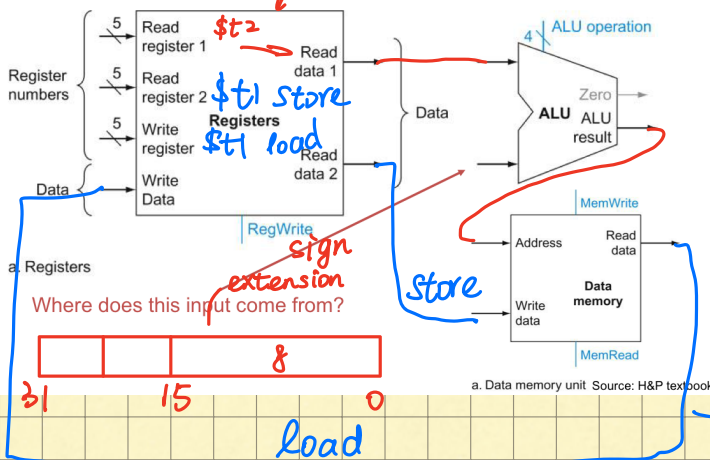


sign extension



下降沿获取数据.

Implementing Cond-Branch Instructions

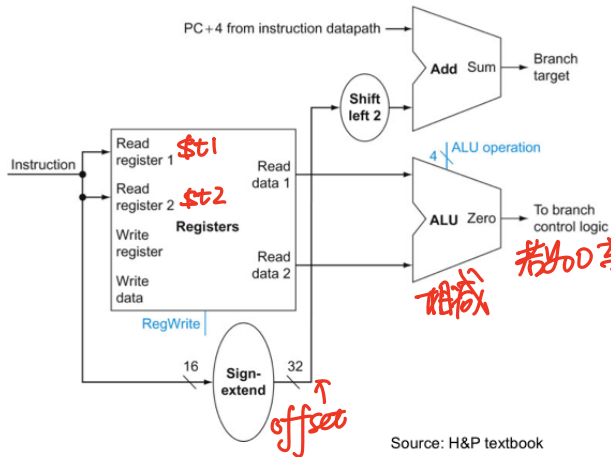
- Instructions of the form `beq $t1, $t2, offset`




若为0则输出1, 否则0.

相减

offset

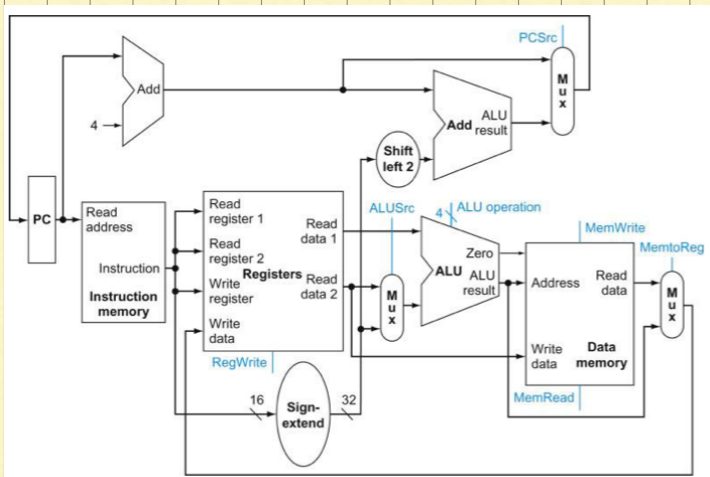

Source: H&P textbook

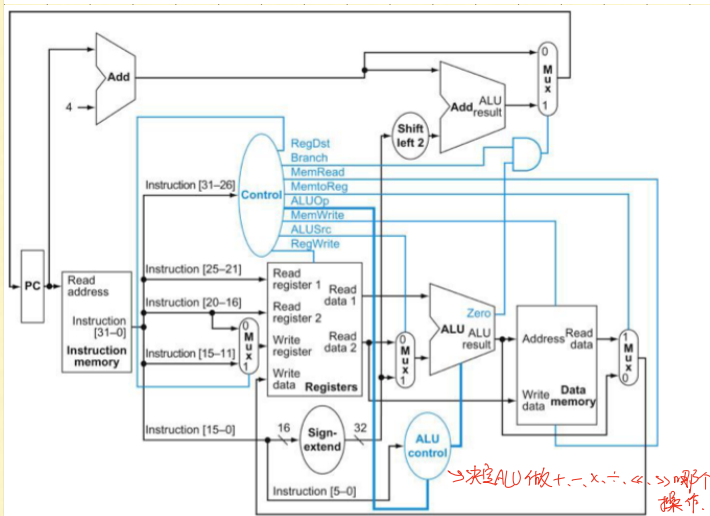

决定ALU做+, -, x, ÷, <, >哪个操作.

Source: H&P textbook